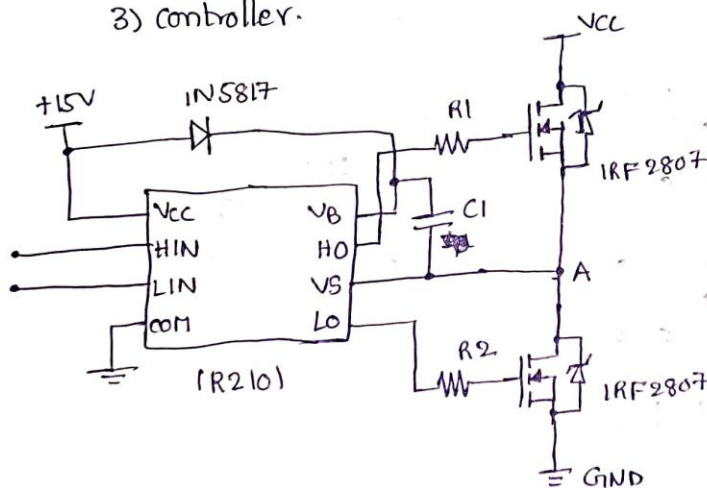


BLDC Motor driver circuit

- * BLDC motor have three-phase windings
- * A driver circuit energizes the correct windings at the right time to maintain rotation.

circuit stages:-

- 1) power stage
- 2) Gate Driver
- 3) controller.



Half bridge with N-channel mosfet


- * The IR2101 provides the gate signals to turn the MOSFETs 'on' and 'off'
- * IR2101 uses a bootstrap capacitor + diode to generate gate voltage higher than the supply.
This allows the high-side MOSFETs to switch properly.

* LO pin of IR2101 directly drives the low-side MOSFETS

MCU

* Arduino generates 6 PWM signal
(HIN + LIN for each IR2101)

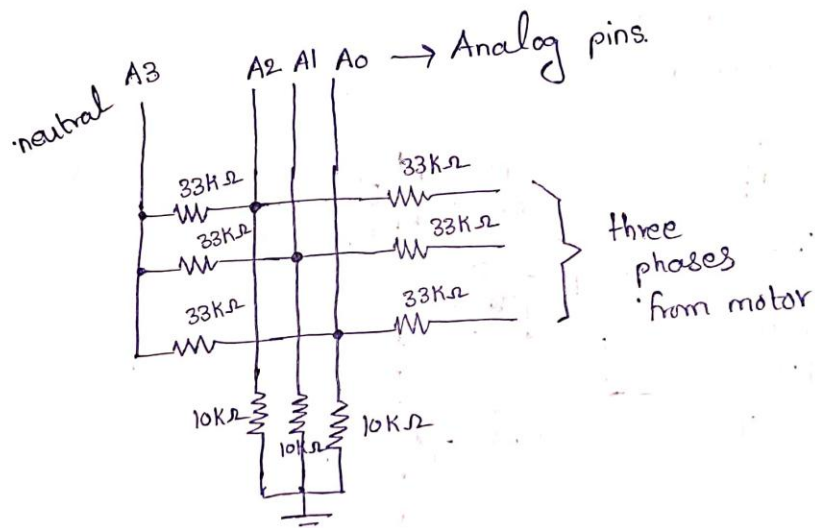pins (11, 10, 9, 6, 5, 3) → generates PWM signals.



$$V_{out} = V_{in} \times \frac{10k\Omega}{30k\Omega + 10k\Omega} = V_{in} \times \frac{10}{40}$$

$$V_{out} \approx 0.25 \times V_{in}$$


* if motor powered by 12V

Arduino sees $\approx 2.8V$

not safe for 24V and 48V, we have to choose more R value.

- * when a phase is floating, Arduino reads its scaled back-EMF waveform
- * Arduino compares this waveform with half of the DC bus voltage (Neutral)
- * when the back-emf crosses this midpoint (zero crossing detection), it means the rotor has reached the right spot

BLDC

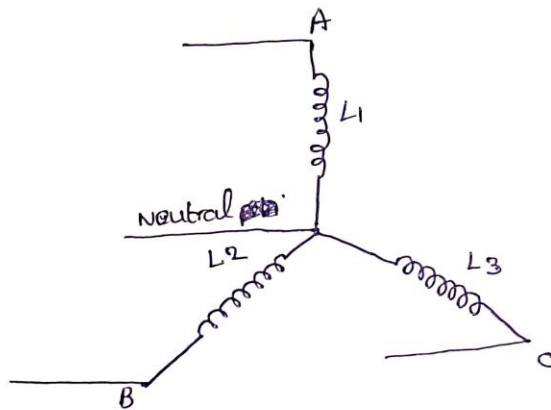

step	1	2	3	4	5	6
High	A	B	B	C	C	A
Low	C	C	A	A	B	B

Windings - Maxed

