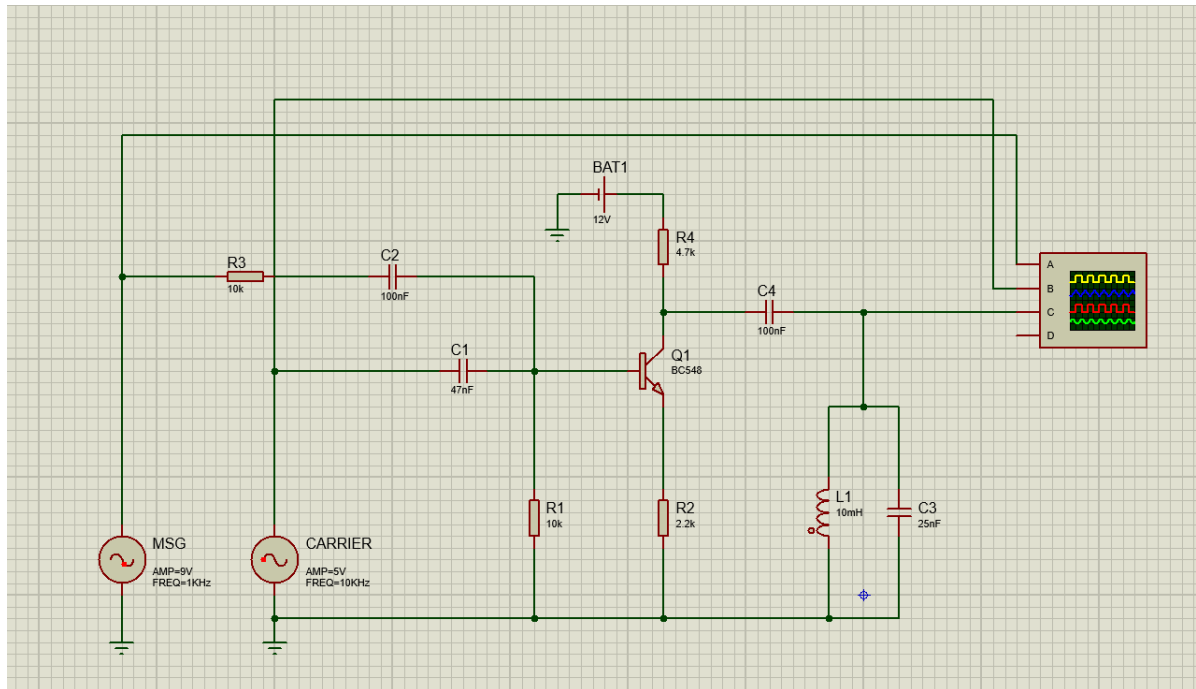



Analog Signal and Digital Signal

Aim: To design two circuits for Analog Signal and Digital Signal


Circuit Diagram for Analog Signal: Amplitude Modulation




Output:

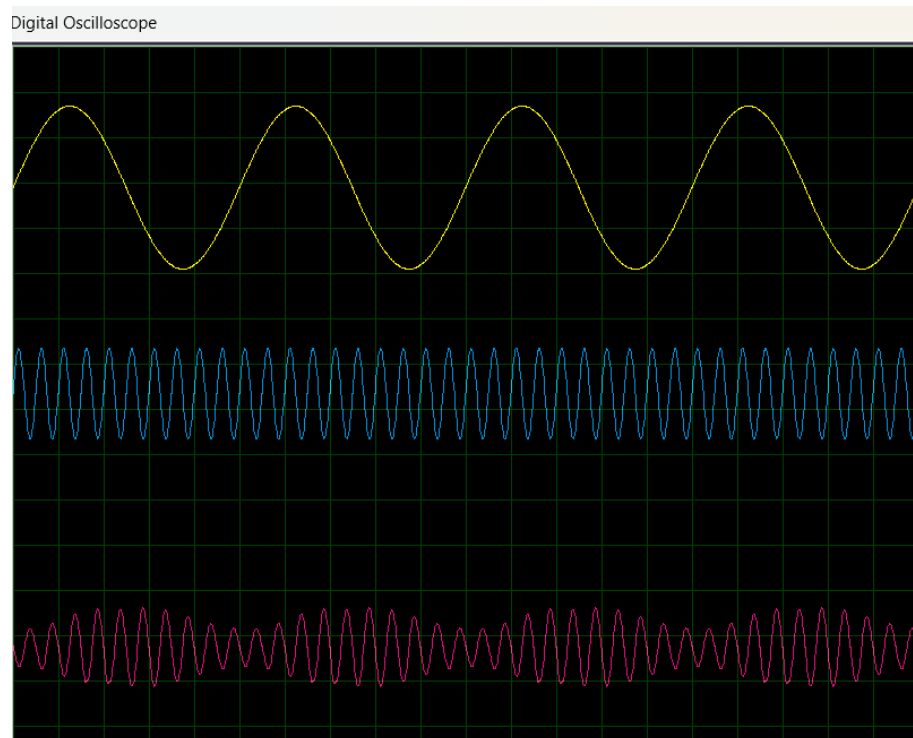

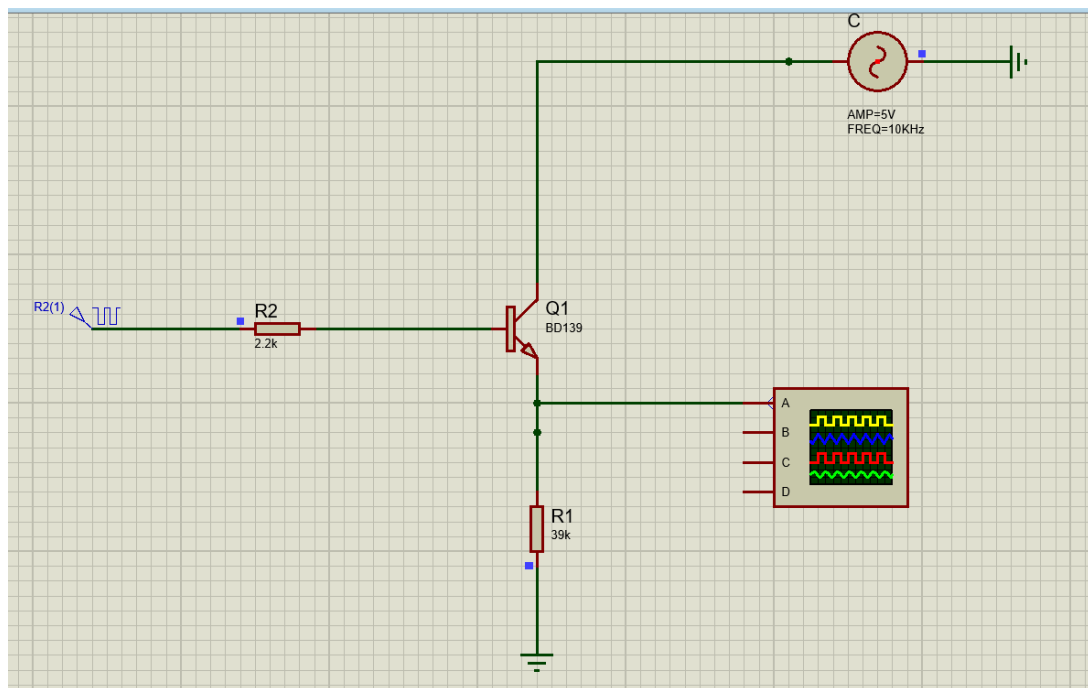Circuit Diagram for Digital Signal: Amplitude Shift keying



Output:

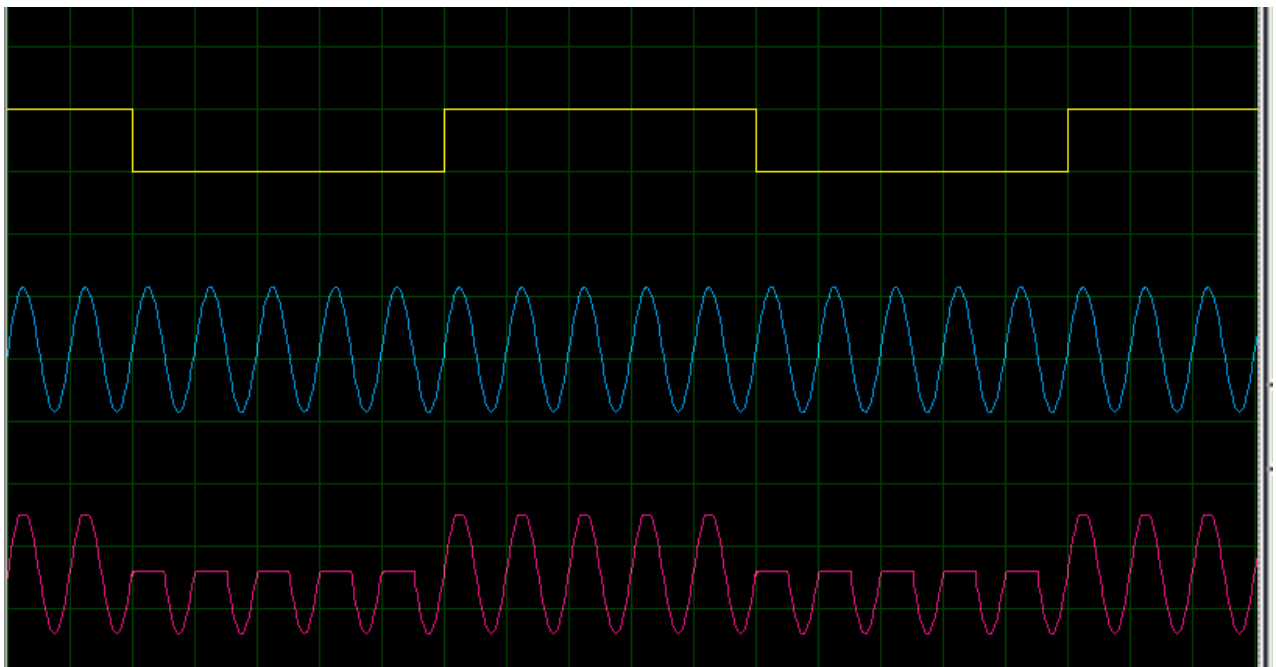

Theory:

Amplitude modulation:-

BC548 transistor is class C amplifier configuration

~~msg~~ → ~~carrier~~

carrier → 10KHz, 5V

msg → 1KHz, 9V

→ high efficiency
→ Suitable for LC tank

BC548 amplifies and modulates the carrier by varying its amplitude according to the message signal.

L1-C3 tank circuit → acts as filter + frequency selector for carrier frequency

output at collector

$R_1 \rightarrow 10K\Omega$ → Base bias resistor

$R_2 \rightarrow 2.2K\Omega$ → emitter resistor → negative feedback

$R_3 \rightarrow 10K\Omega$ → Limit current of modulating (msg) signal

$R_4 \rightarrow 4.7K\Omega$ → collector load resistor

$$\text{Gain} \approx \frac{R_C}{R_E} = \frac{R_4}{R_2} = \frac{4.7K\Omega}{2.2K\Omega} \approx 2.13 \rightarrow \text{sufficient for low power AM.}$$

$R_4 \rightarrow$ if too large → output clipped

$R_4 \rightarrow$ if too small → weak signal

4.7K Ω is optimum

Resonate frequency of tank circuit

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(10mH)(25nF)}} \approx 10KHz$$

ASK

ASK is a modulation technique where the amplitude of a carrier wave is varied according to a digital input signal (0 or 1)

$$R_2 = 2.2 \text{ K}\Omega$$

→ controls base current to switch Q1 fully ON without damaging it.

$$\rightarrow I_B = \frac{I_C}{\beta}$$

β is current gain.

β for BD139, typically 40-100

$$V_{in} = 5V, \beta = 50$$

$$V_{BE} \approx 0.7V,$$

$$\text{Desired } I_C = 10 \text{ mA}$$

R1 is pull down resistor

$$I_B = \frac{10 \text{ mA}}{50} = 0.2 \text{ mA}$$

BD139 is very high frequency Transistor

$$R_2 = \frac{V_{in} - V_{BE}}{I_B} = \frac{5V - 0.7V}{0.2 \text{ mA}} \approx 21.5 \text{ K}\Omega$$

But $2.2 \text{ K}\Omega$ is used for safety

overdrives the base to ensure saturation under any condition.

R_2 ensures the reliable switching and protect the base

the mathematical representation of ASK is

$$s(t) = [m(t) \cdot A_c] \cos(2\pi f_c t)$$